

ASSIGNMENT-1

SNEHA SINGHAL

26-05-2019

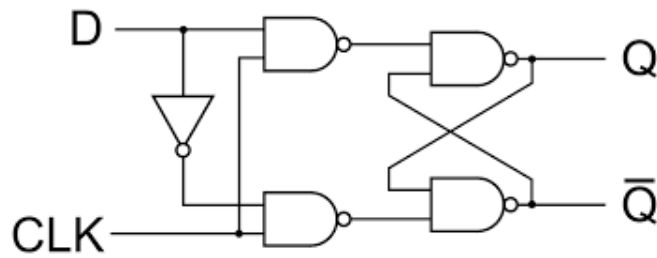


Figure 1: D flipflop circuit

1 QUESTIONS

1.1 Design a 3 bit up counter using D flipflop. Display the output on LEDs.

LOGIC FUNCTION

```
#include "Arduino.h"
int dff(int D)
{
    int S,R,Q=0,NQ=1,s,r,CK=1;
    S=D;
    R=!D;
    s=!(CK&&S);
    r=!(CK&&R);
    Q=!(s&&NQ);
    NQ=!(r&&Q);
    return Q;
}
```

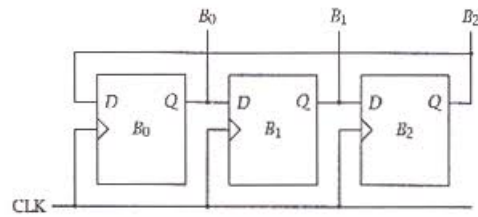


Figure 2: 3 bit Up Counter Circuit

PROGRAM

```
#include "Arduino.h"
#include "dff.h"
int A,B,C,E,F,G;
void setup()
{
  pinMode(6,OUTPUT);
  pinMode(7,OUTPUT);
  pinMode(8,OUTPUT);
  Serial.begin(9600);
}
void loop()
{
  A=0;
  B=0;
  C=0;
  for(int i=1;i<=8;i++)
  {
    E=dff(A);
    F=dff(B);
    G=dff(C);
    Serial.println(E);
    digitalWrite(6,E);
    digitalWrite(7,F);
    digitalWrite(8,G);
    delay(1000);
    if(i%4==0)
      A=!A;
    if(i%2==0)
      B=!B;

    C=!C;
  }
}
```

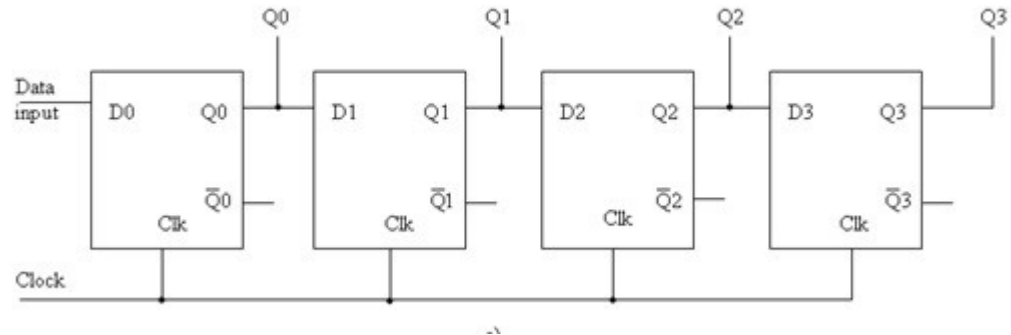


Figure 3: 4 bit Up Counter Circuit

1.2 Design a 4 bit up counter using D flipflop. Display the output on SSD using 7447 IC

PROGRAM

```
#include "Arduino.h"
#include "dff.h"
int A,B,C,E,F,G,H,Z;
void setup()
{
  pinMode(6,OUTPUT);
  pinMode(7,OUTPUT);
  pinMode(8,OUTPUT);
  pinMode(9,OUTPUT);
  Serial.begin(9600);
}
void loop()
{
  A=0;
  B=0;
  C=0;
  Z=0;
  for(int i=1;i<=10;i++)
  {
    E=dff(A);
    F=dff(B);
    G=dff(C);
    H=dff(Z);
    Serial.println(E);
    digitalWrite(6,H);
    digitalWrite(7,G);
    digitalWrite(8,F);
```

```
    digitalWrite(9,E);  
    delay(1000);  
    if (i%8==0)  
    A=!A;  
    if (i%4==0)  
    B=!B;  
    if (i%2==0)  
    C=!C;  
  
    Z=!Z;  
  }  
}
```